 


Lab 5


1. $SOUT = A \text{ xor } B \text{ xor } CIN$
 $COUT = AB + (A \text{ xor } B)CIN$

2.



 3.

4 gates are on the path from inputs to C2



4.

```
module myfulladd(input a, b, cin, output sout, cout);
    assign sout = (a^b^cin);
    assign cout = ((a^b&cin) | (a&b));
endmodule
```
5.

```
module myadder2(input a1, a0, b1, b0, c0, output s1, s0, c2);
    wire c1;
    myfulladd(a1, a0, c0, s0, c1);
    myfulladd(b1, b0, c1, s1, c2);
endmodule
```
6.
 - i. Test A1 = 0 and A0, B1, B0 = 1. This is the only time where C2 should equal 1 when A1 = 0.
 - ii. To test the individual carry connections, use an intermediate output C1 and set it equal to COUT. Observe if C1 is the same as CIN.
 - iii. Basic test for functionality is to set all input to 1. Expect to see S1 and C2 equal to 1 and S0 equal to 0.
 - iv. Keep one of the 2 sets of inputs constant. Vary the other two to observe if the output is correct. If not, change the wiring on the affected adder.

Lab


```
module myadder4(X, Y, C0, V, S, C4);
    input [3:0] X, Y;
    input C0;
    output [3:0] S;
    output V, C4;

    wire C[3:1];

    myfulladder a1(X[0], Y[0], C0, S[0], C[1]);
    myfulladder a2(X[1], Y[1], C[1], S[1], C[2]);
    myfulladder a3(X[2], Y[2], C[2], S[2], C[3]);
    myfulladder a4(X[3], Y[3], C[3], S[3], C4);

    assign V = C[3]^C4;
endmodule

module myfulladder(input a, b, cin, output sout, cout);
    assign sout = (a^b^cin);
    assign cout = ((a&b)|(b&cin)|(a&cin));
endmodule
```

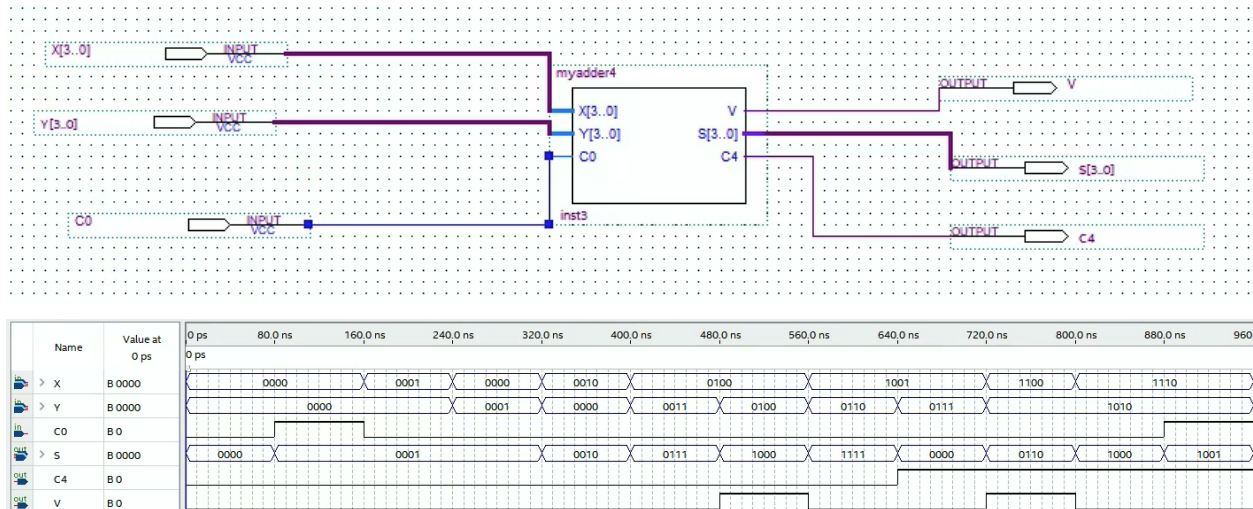

- C4 = 0 and V = 0 when X = 0 and Y = 0

C4 = 0 and V = 1 when X = 4 and Y = 4

C4 = 1 and V = 0 when X = 9 and Y = 7

C4 = 1 and V = 1 when X = C and Y = A
- To make an 8 bit adder, I would connect the C4 of one 4 bit adder to C0 of the other 4 bit adder. The new V output would be C8^C7 and the C8 output would be created from the second 4 bit adder as well as the carry in of the first 4 bit adder.
- The initial testing of the circuit went smoothly.
- No this would not be caught because since it is an adder, these bits would still be added anyways since they are of the same magnitude.
- The incorrect results are shown when adding A=2 & B = 1, A = 0 & B = 11, A = 3 & B = 9, A = 1 & B = 9, A = 7 & B = 4, and A = 11 & B = 0
 - It looks like the error is in the wiring of A as shown by tests 6 & 7 (A = 3, 1 and B = 9). Since for the same B input, the outputs are incorrect.
 - To address this, more extensive tests on A would need to be done. To identify which bit is misbehaving, I would test all possible combinations of A (16 tests total).